

Y4 D & T Knowledge Organiser - Alarms

How do I make an alarm?



Vocabulary

Prototype - The first example/model

Electrical circuit - A complete circuit lets electricity flow through

Switch - an on switch (closed) lets electricity through, an off switch (open) doesn't let electricity through